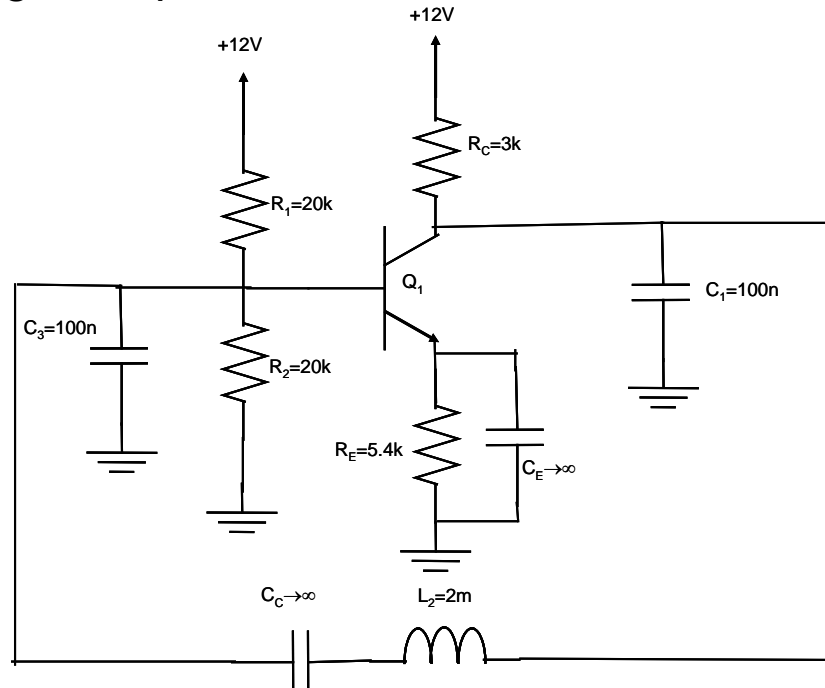




Exercise:

The figure represents the circuit of a sinusoidal oscillator:



Q_1 Data:

$$V_{BEact}=0.6V$$

$$V_{CEsat}=0.2V$$

$$\beta=160$$

$$V_T=25mV$$

$$r_o \rightarrow \infty$$

$$C_\mu = 0$$

$$C_\pi = 0$$

- Indicate what type of oscillator it is and identify the networks A^* and β^* .
- Obtain the operating point in DC of Q_1 .
- Obtain the generic equivalent circuit (input resistance, voltage gain and output resistance) in small signal at medium frequencies of network A^* . (If you have not resolved the previous section, consider $I_{CQ1} = 1mA$).
- Obtain the expression of the loop gain ($A^* \cdot \beta^* (j\omega)$) of the oscillator, justifying the approximations made in the calculations.
- Deduce the value of the oscillation angular frequency (ω_{osc}) of the circuit.
- Would the oscillator start with the values of the components given in figure 3? Justify your answer.